

ENGR 210 / CSCI B441
“Digital Design”

SPI I *Test*

Andrew Lukefahr

Announcements

- P8 – Elevator Controller is out

- This one is hard.

due Friday

- P9 – SPI is out

→ Last One

- This one is new. Might be some changes.

until E315

- The end is in sight...

for(;;) Loops in Verilog

- Testbenches – just like C/C++
- Synthesizable modules - more like #define



Always specify
defaults for
always_comb!

BLOCKING (=) FOR

always_comb

NON-BLOCKING (<=) for


always_ff

Lock State Machine



- Recall: 5 - 4 - 3


- E: relock

 

State Machine in Verilog

```
module Lock(  
    input clk, rst,  
    input [9:0] num,  
    input e, //relock  
    output unlock  
) ;
```
 
```
enum {ST_IDLE, ST_5, ST_4, ST_UL} state, next_state;  
  
//seq logic  
always_ff @(posedge clk) begin  
    if (rst) state <= ST_IDLE;  
    else      state <= next_state;  
end
```




~~Fixme~~ ~~misses~~ \rightarrow misses the default stuff of State Machine in Verilog

```

case (state)
    ST_IDLE:
        if (num[5])
            next_state = ST_5;
    ST_5: begin
        if (num[4])
            next_state = ST_4;
        else if (num[5])
            next_state = ST_5;
        else if ((|num) | e) //other btns
            next_state = ST_IDLE;
    end
    ST_4: begin
        if (num[3])
            next_state = ST_UL;
    end
endcase

```

 


```


        else if (num[5])
            next_state = ST_5;
        else if ( (|num) | e) // other btns
            next_state = ST_IDLE;
    end
    ST_UL: begin
        unlock = 1'h1;
        if (e)
            next_state = ST_IDLE;
    end
endcase

```

Glitch


 


 Results in a short low-going pulse at the output of N_2 with length approximately equal to the propagation delay through N_1 .





Flip-Flop Timing

- Assume 5ps/ Gate

  

Flip-Flop Timing


- Assume 5ps/ Gate

  


Setup and Hold Time

- **Setup Time:** minimum time the inputs to a flip-flop must be stable before the clock edge
- **Hold Time:** minimum time the inputs to a flip-flop must be stable after the clock edge


Setup/Hold Time

 


Setup/Hold Time

 

Intra Flip-Flop Timing

 


Inter Flip-Flop Timing

 

Intra Flip-Flop Timing

Register to register timing:

 - output of a register $Q1$
- some combinational circuit
- input to the next register $D2$




Delays:

- t_{co} , clock to output delay,
- t_{pd} , propagation delay in combinational circuit
- t_c , clock period

Timing requirement:


$$t_{co} + t_{pd} + t_{su} < t_c$$

 

Slack

- Extra time between combinational propagation delay and setup time
- Time between stable input to Flip-Flop and next clock edge

 - Vivado:
 - WNS: Worst-case Negative Slack



- If this number is <0, your circuit will (probably) not work

for(;;) Loops in Verilog

- Testbenches – just like C/C++
- Synthesizable modules - more like #define

for(;;) Loops in Verilog

- Testbenches – just like C/C++
- Synthesizable modules - more like #define
- `for(;;)` loop is expanded at **Compile (Synthesis) Time**

Correct for (;;) Loops in Verilog


```
module MysteryFunction (
    input[3:0] a,
    input[1:0] right,
    output[3:0] y
);
    //correct for loop
    integer x; // OR genvar x
    for (x = 0; x < 4; x++) begin
        assign y[x] = a[x+right];
    end
endmodule
```

assign y[0]=a[right];
" y[1]=a[1+right];
y[2]=a[2+right],
y[3]=a[3+right],

Correct for (;;) Loops in Verilog

```
module RightBarrelShift (
    input[3:0] a,
    input[1:0] right,
    output[3:0] y
);
```
 
```
{ //correct for loop
    integer x; // OR genvar x
    for (x = 0; x <= 4; x++) begin
        assign y[x] = a[x+right]; →
    end
} endmodule
```



assign $y[0] = a[0 + \text{right}]$
assign $y[1] = a[1 + \text{right}]$
...

Correct for (;;) Loops in Verilog

This Code:

```
integer x; //or genvar x
for (x = 0; x < 4; x++) begin
    assign y[x] = a[x+right];
end
```

Expands to:

```
assign y[0] = a[0 + right];
assign y[1] = a[1 + right];
assign y[2] = a[2 + right];
assign y[3] = a[3 + right];
```

Incorrect for (;;) Loops in Verilog

```
integer i;  
wire carry;  
  
for(i = 0; i < 4; i++) begin  
    if (i == 0) begin  
        assign sum[i] = a[i] ^ b[i] ^ c_in;  
        assign carry = a[i] & b[i] | a[i] & c_in | b[i] & c_in;  
    end else begin  
        assign sum[i] = a[i] ^ b[i] ^ carry;  
        assign carry = a[i] & b[i] | a[i] & carry | b[i] & carry;  
    end  
end  
assign c_out = carry;
```

What is wrong here?


Incorrect for (;;) Loops in Verilog

```
integer i;  
wire carry;  
  
for(i = 0; i < 4; i++) begin  
    if (i == 0) begin  
        assign sum[i] = a[i] ^ b[i] ^ c_in;  
        assign carry = a[i] & b[i] | a[i] & c_in | b[i] & c_in;  
    end else begin  
        assign sum[i] = a[i] ^ b[i] ^ carry;  
        assign carry = a[i] & b[i] | a[i] & carry | b[i] & carry;  
    end  
end  
assign c_out = carry;
```

What is wrong here?

Incorrect for (;;) Loops in Verilog

```
integer i;  
wire carry[3:0];  
  
assign sum[0] = a[0] ^ b[0] ^ c_in;  
assign carry[0] = a[0] & b[0] | a[0] & c_in | b[0] & c_in;  
  
assign sum[1] = a[1] ^ b[1] ^ carry[1];  
assign carry[1] = a[1] & b[1] | a[1] & carry[0] | b[1] & carry[0];  
  
assign sum[2] = a[2] ^ b[2] ^ carry[2];  
assign carry[2] = a[2] & b[2] | a[2] & carry[1] | b[2] & carry[1];  
  
assign sum[3] = a[3] ^ b[3] ^ carry[3];  
assign carry[3] = a[3] & b[3] | a[3] & carry[2] | b[3] & carry[2];  
  
assign c_out = carry;
```

 

Correcting for (;;) Loops in Verilog

```
integer i;  
wire carry;  
  
for(i = 0; i < 4; i++) begin  
    if (i == 0) begin  
        assign sum[i] = a[i] ^ b[i] ^ c_in;  
        assign carry = a[i] & b[i] | a[i] & c_in | b[i] & c_in;  
    end else begin  
        assign sum[i] = a[i] ^ b[i] ^ carry;  
        assign carry = a[i] & b[i] | a[i] & carry | b[i] & carry;  
    end  
end  
assign c_out = carry;
```

How do we fix this?

Correcting for (;;) Loops in Verilog

```
integer i;  
wire [3:0] carry;  
  
for(i = 0; i < 4; i++) begin  
    if (i == 0) begin  
        assign sum[i] = a[i] ^ b[i] ^ c_in;  
        assign carry[i] = a[i] & b[i] | a[i] & c_in | b[i] & c_in;  
    end else begin  
        assign sum[i] = a[i] ^ b[i] ^ carry[i-1];  
        assign carry[i] = a[i] & b[i] | a[i] & carry[i-1] | b[i] & carry[i-1];  
    end  
end  
assign c_out = carry[3];
```


How do we fix this?

Correcting for (;;) Loops in Verilog

```
integer i;  
wire carry;  
  
assign sum[0] = a[0] ^ b[0] ^ c_in;  
assign carry[0] = a[0] & b[0] | a[0] & c_in | b[0] & c_in;  
  
assign sum[1] = a[1] ^ b[1] ^ carry[0];  
assign carry[1] = a[1] & b[1] | a[1] & carry[0] | b[1] & carry[0];  
  
assign sum[2] = a[2] ^ b[2] ^ carry[1];  
assign carry[2] = a[2] & b[2] | a[2] & carry[1] | b[2] & carry[1];  
  
assign sum[3] = a[3] ^ b[3] ^ carry[2];  
assign carry[3] = a[3] & b[3] | a[3] & carry[2] | b[3] & carry[2];  
  
assign c_out = carry[3];
```

Serial Communication

- Do you remember this circuit?


 


- What did it do?


shift register,
shift in data
Convert serially
to parallel

Converts serial input to parallel output

Shift Register

  


What does this circuit do?

 

circular shifter

What about this circuit?

 


MOSI: Master Out Slave In
Serial Data Out (SDO)

MISO: Master In Slave Out
Serial Data In (SDI)

Serial Peripheral Interface (SPI)

- The **Serial Peripheral Interface (SPI)** is a synchronous **serial communication interface** specification used for short-distance communication, primarily in embedded systems.
- SPI devices **communicate in full duplex** mode using a master-slave architecture. The master (controller) device **originates the frame for reading and writing**. Multiple slave-devices may be supported through selection with individual chip select (CS), sometimes called slave select (SS) lines.
- [Wiki]

SPI

 




SCK


CLOCK

MOSI

DATA

 


When to CAPTURE new data?

 



When to SEND new data?

④ falling edge of
SCK

 


SPI Example

Master

  

Next Time

 - clk vs CLOCK [00MHz vs, SCK] 

CLK
SCK
- Synchronizers